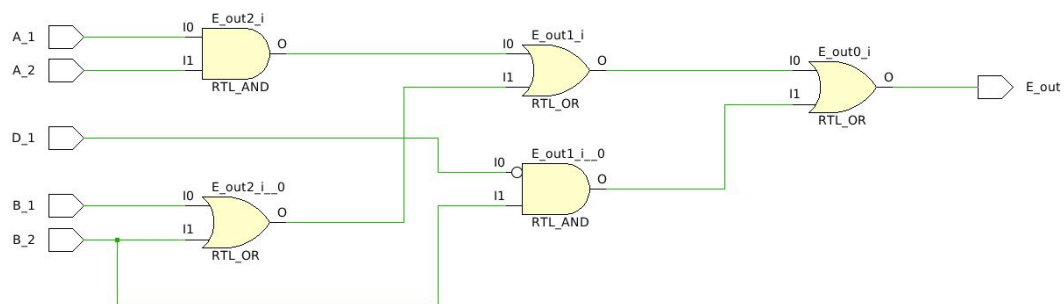


TIMOTHY LANGER
EMBEDDED SYSTEMS
RUID 189005424
HW #5
2)

IF STATEMENTS:

SCHEMATIC:



CODE:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity if_ckt is
    Port ( A_1 : in STD_LOGIC;
          A_2 : in STD_LOGIC;
          B_1 : in STD_LOGIC;
          B_2 : in STD_LOGIC;
          D_1 : in STD_LOGIC;
          E_out : out STD_LOGIC);
end if_ckt;
```

architecture Behavioral of if_ckt is

begin

process (A_1, A_2, B_1, B_2, D_1)

begin

if((A_1 and A_2) ='1' or (B_1 or B_2)='1' or ((not D_1) and B_2)='1')then
 E_out <='1';

else


E_out <='0';

end if;

end process;

end Behavioral;

CASE STATEMENTS

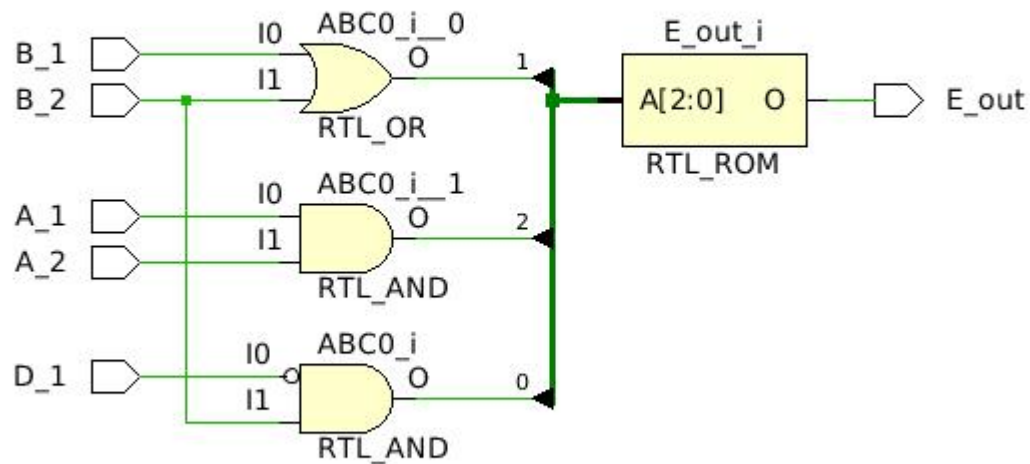

CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity case_ckt is
    Port ( A_1 : in STD_LOGIC;
          A_2 : in STD_LOGIC;
          B_1 : in STD_LOGIC;
          B_2 : in STD_LOGIC;
          D_1 : in STD_LOGIC;
          E_out : out STD_LOGIC);
end case_ckt;

architecture Behavioral of case_ckt is
    signal A_out, b_out, C_out : std_logic;
    signal ABC : std_logic_vector (2 downto 0);

begin
```

```
ABC <= A_out & B_out & C_out;
```

```
process (A_1, A_2, B_1, B_2, D_1)  
begin
```

```
A_out <= A_1 and A_2;
```

```
B_out <= B_1 or B_2;
```

```
C_out <= (not D_1) and B_2;
```

```
case (ABC) is
```

```
when "000" => E_out <= '0';
```

```
when "001" => E_out <= '1';
```

```
when "010" => E_out <= '1';
```

```
when "011" => E_out <= '1';
```

```
when "100" => E_out <= '1';
```

```
when "101" => E_out <= '1';
```

```
when "110" => E_out <= '1';
```

```
when "111" => E_out <= '1';
```


```
end case;
```

```
end process;
```

```
end Behavioral;
```

3) Using Concurrent signal assignment to implement the same circuit

SCHEMATIC:

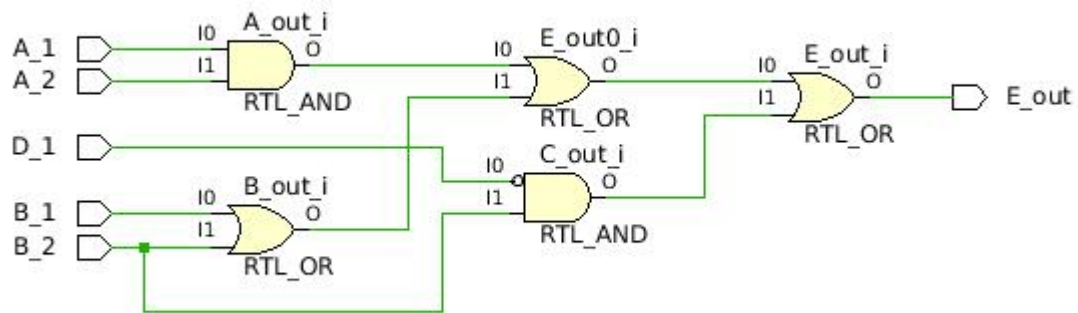

CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity concurrent_design is
    Port ( A_1 : in STD_LOGIC;
          A_2 : in STD_LOGIC;
          B_1 : in STD_LOGIC;
          B_2 : in STD_LOGIC;
          D_1 : in STD_LOGIC;
          E_out : out STD_LOGIC);
end concurrent_design;
```

architecture Behavioral of concurrent_design is

```
    signal A_out, B_out, C_out : std_logic;
```

```
begin
```


```
    A_out <= A_1 and A_2;
    B_out <= B_1 or B_2;
    C_out <= (not D_1) and B_out;
    E_out <= A_out or B_out or C_out;
```

```
end Behavioral;
```

6) 8 to 1 Multiplexer

USING CASE STATEMENTS:

SCHEMATIC:

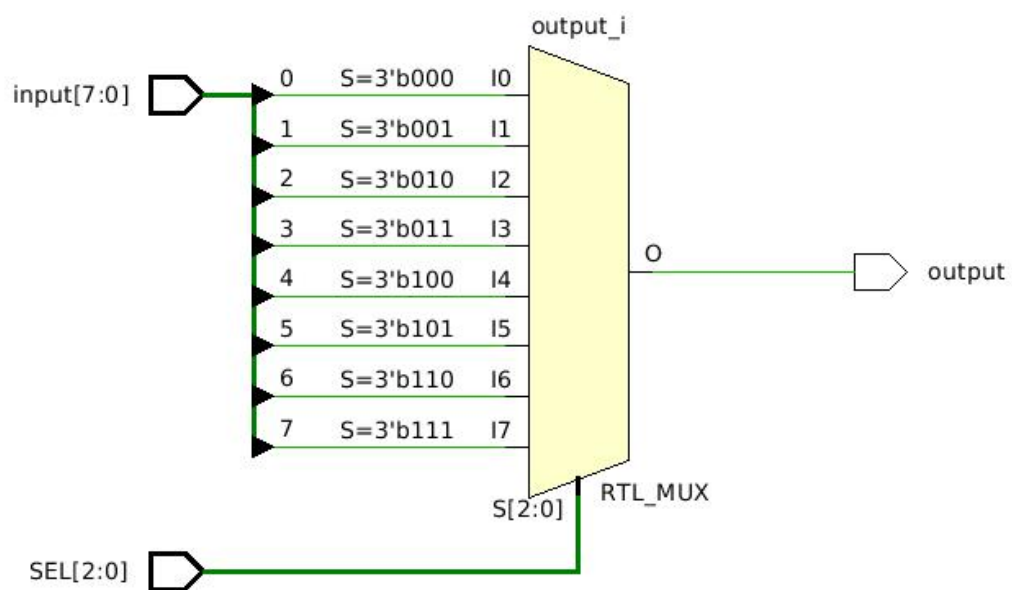

(VHDL CODE ON NEXT PAGE)

VHDL CODE:

```
library IEEE;
use IEEE.std_logic_1164.all;

entity mux is
port (
input : in std_logic_vector (7 downto 0);
SEL : in std_logic_vector (2 downto 0);
output : out std_logic);
end mux;


architecture behavioral of mux is
begin

process (SEL,input)
begin

case (SEL) is
when "000" => output <= input(0);
when "001" => output <= input(1);
when "010" => output <= input(2);
when "011" => output <= input(3);
when "100" => output <= input(4);
when "101" => output <= input(5);
when "110" => output <= input(6);
when "111" => output <= input(7);
when others => output <= '0';
end case;
end process;
end behavioral;
```

8 to 1 mux, USING IF STATEMENTS:

SCHEMATIC:

 

CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity if_mux is
    Port ( input : in STD_LOGIC_VECTOR (7 downto 0);
          SEL : in STD_LOGIC_VECTOR (2 downto 0);
          output : out STD_LOGIC);
end if_mux;

architecture Behavioral of if_mux is

begin

    process (SEL,input)
    begin


        if SEL = "000" then output<= input(0);
        elsif SEL = "001" then output<= input(1);
        elsif SEL = "010" then output<= input(2);
        elsif SEL = "011" then output<= input(3);
        elsif SEL = "100" then output<= input(4);
        elsif SEL = "101" then output<= input(5);
        elsif SEL = "110" then output<= input(6);
        elsif SEL = "111" then output<= input(7);
        else
            output<='0';
        end if;

    end process;

end Behavioral;
```

8) DECODER USING CASE:

SCHEMATIC:

 

CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity case_decoder is
    Port ( input : in STD_LOGIC_VECTOR (2 downto 0);
          output : out STD_LOGIC_VECTOR (7 downto 0));
end case_decoder;
```

architecture Behavioral of case_decoder is

```
begin
process(input)
begin
case (input) is
when "000" => output <= "11111110";
when "001" => output <= "11111101";
when "010" => output <= "11111011";
when "011" => output <= "11110111";
when "100" => output <= "11101111";
when "101" => output <= "11011111";
when "110" => output <= "10111111";
when "111" => output <= "01111111";
when others => output <= "11111111";
end case;
end process;
end Behavioral;
```


DECODER USING IF STATEMENTS:

CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity decoder_if is
    Port ( input : in STD_LOGIC_VECTOR (3 downto 0);
          output : out STD_LOGIC_VECTOR (7 downto 0));
end decoder_if;

architecture Behavioral of decoder_if is

begin

    process(input)
    begin
        if input = "000" then output <= "11111110";
        elsif input = "001" then output <= "11111101";
        elsif input = "010" then output <= "11111011";
        elsif input = "011" then output <= "11110111";
        elsif input = "100" then output <= "11101111";
        elsif input = "101" then output <= "11011111";
        elsif input = "110" then output <= "10111111";
        elsif input = "111" then output <= "01111111";
        else output <= "11111111";
        end if;

    end process;

end Behavioral;
```